

EXPERIMENT - 4

PROGRAMMABLE GAIN AMPLIFIER

GROUP NO: W11

MEMBERS:

- 1) PUNUMALLI KARTHIK — 180102052
- 2) NELAPATI LOKESH — 180102045
- 3) PRASHANTH KHATRI — 180102050

EXPERIMENT-4

PROGRAMMABLE GAIN AMPLIFIER

OBJECTIVE:

To design and implement a programmable gain amplifier (PGA) with the given specifications using analog switch CD4066.

SPECIFICATIONS:

- (i) one analog input
- (ii) one analog output
- (iii) Two TTL control inputs (S_1 and S_2) decide the gain of PGA as follows:

S_1	S_2	Gain
0	0	1
0	1	15
1	0	80
1	1	100


Components needed:

- (i) opamp
- (ii) Resistances of adequate values
- (iii) CD4066 Switch
- (iv) 2N2222A PNP and NPN transistors (2 each)
- (v) wires
- (vi) power supply.


Theory:

- Block diagram of PGA unit with Analog input (V_i), Analog output (V_o) and TTL control inputs (A, B) are provided below.

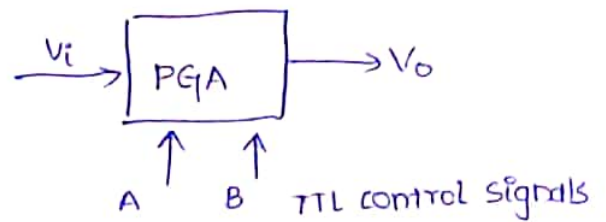- changing the TTL control inputs changes the effective gain (V_o/V_i) making it act like a programmable unit.



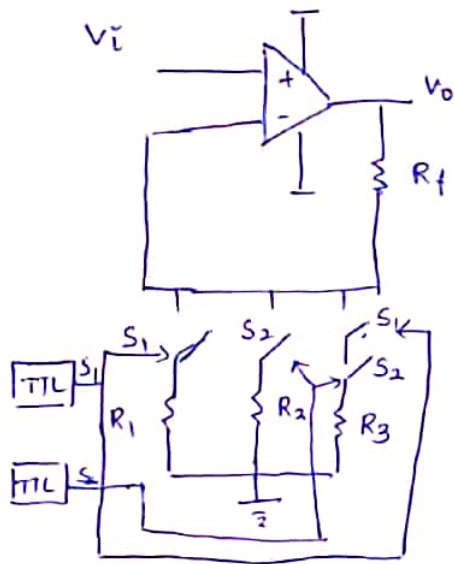- The opamp can be used to design the system with control signals representing switches as shown below.



- The resistances R_1, R_2, R_3 and R_f are designed such that the gain of the system changes as switch S_1, S_2 are turned ON (signal=1) and OFF (signal=0).
- The switch S_1, S_2 and S_3 (combination of S_1 and S_2) are designed using CD4066 switch.


- The CD4066 contains four independent switches. The control signal determines whether switch is 'ON' or 'OFF' when

(i) CONTROL = V_{DD} → switch closed

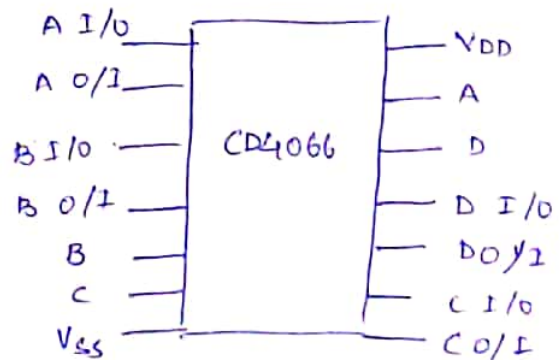(ii) CONTROL = V_{SS} → switch OPEN


Typical R_{ON} of switch $\approx 150\Omega$

Here $SW_A = S_1, SW_D = S_2, SW_B$ and SW_C together is S_3 .



- One problem with CD4066 switch is that it is bipolar and requires control signal to have both positive or negative value available to it while TTL signal are 0 or 5V and as such it requires a level shifter.

* WORKING OF LEVEL SHIFTER:

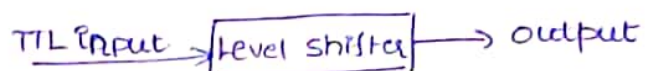

In level shifter when TTL input = 5V (logic = 1), output should be V_{DD} (Here $V_{DD} = 5V$) and when TTL input = 0 (logic = 0) output should be V_{SS} . (Here $V_{SS} = -5V$).

• Designing level shifter using BJT's:

We will use one PNP and NPN transistor to create level shifter for 1 switch

Sat. Specifications for PNP transistor used: $I_C = 10mA$, $I_B = 0.5mA$, $\beta = 20$,

$$V_{BE} = 0.7V \quad V_{CE} = 0.2V$$

Sat. Specifications for NPN transistor used: $I_C = 150mA$, $I_B = 15mA$, $\beta = 10$,

$$V_{BE} = 0.7V, \quad V_{CE} = 0.2V$$


$V_i \rightarrow$ TTL Input

$$V_i = \{0, 5\}V$$

$V_{out} =$ output

voltage to be

used in switch CD4066

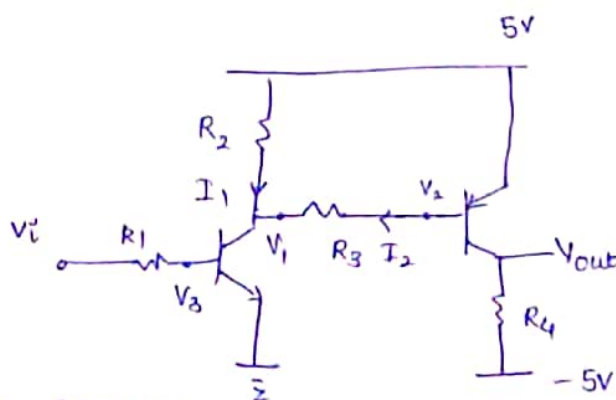

• calculation of R_1, R_2, R_3 and R_4

When $V_i = 5V$ $V_{out} = 4.8V$ ($V_{out} = 5 - V_{CE} \approx 4.8V$)

$$\frac{V_i - V_3}{R_1} = 15mA \Rightarrow \frac{5 - 0.7}{R_1} = 15 \times 10^{-3} \Rightarrow \boxed{R_1 = 286\Omega}$$

$$R_4 = \frac{V_{out}}{I_c} = \frac{9.8}{10 \times 10^{-3}} = 980\Omega \Rightarrow \boxed{R_4 = 980\Omega}$$

$V_1 \approx 0.2V$, $V_2 = V_{out} - V_{BE} = 4.3V$


$$R_3 = \frac{V_2 - V_1}{0.5 \times 10^{-3}} = 8.2k\Omega \Rightarrow \boxed{R_3 = 8.2k\Omega}$$

Also,

$$R_2 = \frac{5 - V_1}{I_1} \approx \frac{5 - V_1}{I_c} = \frac{4.8}{150 \times 10^{-3}} = 32\Omega$$

$$\Rightarrow \boxed{R_2 = 32\Omega}$$

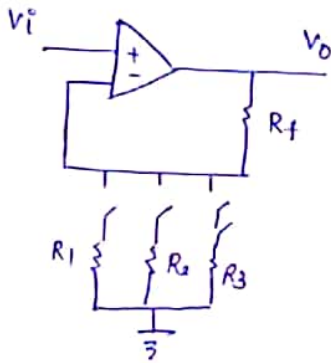• Designing gain circuit (calculating resistances for getting desired gain)



Take $R_{ON} = 150\Omega$

Let $R_f = 100k\Omega$

When $S_1 = S_2 = 0$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i} \approx 1 \quad (R_i \rightarrow \infty)$$

When $S_1 = 0, S_2 = 1$

$$\frac{V_o}{V_i} = 1 + \frac{R_f}{R_2 + 150} = 15$$

When $S_1 = 1, S_2 = 0$

$$1 + \frac{R_f}{R_1 + 150} = 80$$

$$\Rightarrow R_1 = \frac{R_f}{79} - 150$$

$$\Rightarrow \boxed{R_1 \approx 7k\Omega}$$

When $S_1 = S_2 = 1$

$$\frac{V_o}{V_i} = 100 = 1 + \frac{R_f}{(R_1 + 150) \parallel (R_2 + 150) \parallel (R_3 + 150)}$$

$$\Rightarrow \boxed{R_3 \approx 16.52k\Omega}$$


$$\Rightarrow R_2 = \frac{R_f}{14} - 150$$

$$\Rightarrow \boxed{R_2 \approx 1.2k\Omega}$$

- Calculating R_{ON} (Resistance offered by switch at ON) and R_{OFF} (Resistance offered at OFF position)

We will use experimental gain to calculate R_{ON} and R_{OFF} .

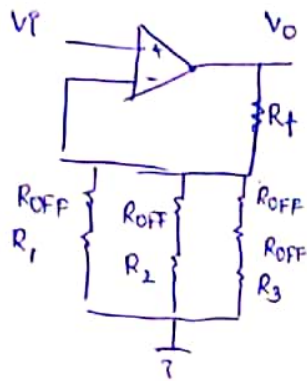When $S_1 = S_2 = 0$ let g_{exp} be experimental (gain \approx)




$$1 + \frac{R_f}{(R_{OFF} + R_1) \parallel (R_{OFF} + R_2) \parallel (R_{OFF} + R_3)} = g_{exp}$$

$$\Rightarrow \frac{R_f}{R_{OFF} \parallel R_{OFF} \parallel 2R_{OFF}} = g_{exp} - 1$$

$$\Rightarrow \boxed{R_{OFF} = \frac{R_f}{0.4 \times (g_{exp} - 1)}}$$

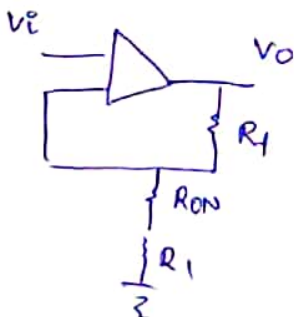When $S_1 = 1, S_2 = 0$ let g_{exp} be experimental gain




$$g_{exp} = 1 + \frac{R_f}{R_{ON} + R_1}$$

$$\boxed{R_{ON} = \frac{R_f}{g_{exp} - 1} - R_1}$$

Department of Electronics & Electrical Engineering
EC207: Analog Circuits Laboratory
Results verification sheet
Experiment No. 4: Programmable Gain Amplifier

Group No. ...W11

1. Circuit Diagram:

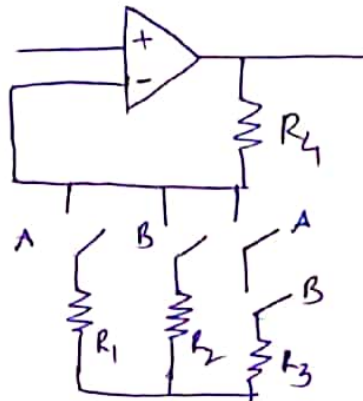

2. Designed value of resistances:

$$R_1 = 7k\Omega \quad R_2 = 1.2k\Omega \quad R_3 = 16.52k\Omega \quad R_4 = 100k\Omega$$

3. Measured value of resistances:

$$R_1 = 6.93k\Omega \quad R_2 = 1.1k\Omega \quad R_3 = 16.48k\Omega \quad R_4 = 99.5k\Omega$$

4. Minimum voltage required to turn on the switch =4.6V.....

Minimum voltage required to turn off the switch =-2.9V.....

5. Measured value of ON resistance of an analog switch, R_{ON} =165 Ω

Measured value of OFF resistance of an analog switch, R_{OFF} =11M Ω

Control Inputs (TTL)		Analog Input (v_i)	Analog Output (v_o)	Gain (v_o/v_i)	Expected Gain
A	B				
0	0	527 mV _{pp}	549 mV _{pp}	1.03	1
0	1	61.3 mV _{pp}	825 mV _{pp}	13.45	15
1	0	64.1 mV _{pp}	4.94 V _{pp}	77.34	80
1	1	64.1 mV _{pp}	6.13 V _{pp}	95.6	100

Signature of the TA

[Signature]

Date 19.02.2020